

Module - II

Solⁿ of First and Second order network:

The circuit that contain capacitors and inductors can be represented by differential equations. If a circuit contain one resistor and one inductor (or one inductor) it can be represented by a first order differential equation. If the circuit contain resistor, inductor and capacitor it can be represented by a second order differential equation. That is the order of the differential equation of a circuit depends on the number of different energy storage elements that it contains. The solⁿ of the differential equation represents the response of the circuit.

In general the response consists of two parts.

- ① Natural response (Transient response)
- ② Forced response (Steady state response)

$$\begin{aligned} \text{Total response} &= \text{Transient response} + \text{Steady state response} \\ &= \text{Natural response} + \text{forced response} \end{aligned}$$

Transient response: The value of voltage and current during the transient period are known as transient response is natural response

Steady state response: The value of voltage and current after the transient has died out are known as steady state response

Differential Equations

Type-I (First order Homogeneous differential equation)

$$\frac{dy(t)}{dt} + py(t) = 0$$

solⁿ of diff. equⁿ,

$y(t) = Ke^{-pt}$

$\Rightarrow \frac{dy(t)}{dt} = -py(t)$
 $\Rightarrow \ln y(t) = -pt + K$
 $K = \ln k$
 $\Rightarrow \ln y(t) = -pt + \ln k$
 $y(t) = k e^{-pt}$

Type-II (First order Non homogeneous Diff. equⁿ)

$$\frac{dy(t)}{dt} + py(t) = Q$$

solⁿ of the above equⁿ, diff.

$y(t) = \frac{Q}{p} + Ke^{-pt}$

Type-III (Second order diff. equation)

$$A \frac{d^2 y(t)}{dt^2} + B \frac{dy(t)}{dt} + C y(t) = 0$$

solⁿ of the above equⁿ,

$y(t) = K_1 e^{p_1 t} + K_2 e^{p_2 t}$

where p_1, p_2 are the roots of the quadratic eq


$$AP^2 + BP + C = 0$$

$$p_1, p_2 = \frac{-B}{2A} \pm \frac{1}{2A} \sqrt{B^2 - 4AC}$$

⑧
If $r_1 = r_2$, roots of the quadratic equation are repeated, then the general solⁿ of the 2nd order diff. eqn.

$$y(t) = k_1 e^{r_1 t} + k_2 t e^{r_1 t}$$

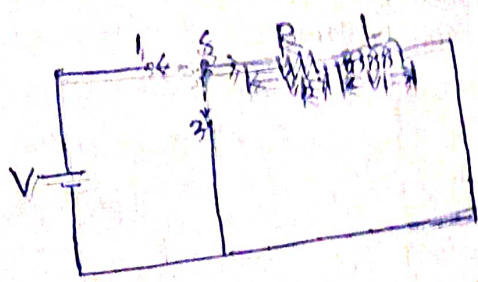GROWTH OF CURRENT IN AN INDUCTIVE CIRCUIT (D.C. TRANSIENT)



Let us consider that a circuit having a resistance R and an inductance L connected to a d.c. voltage V as shown. The R-L combination becomes connected to ^{d.c.} potential voltage source when switch S is connected to terminal '1' and is short circuited when 'S' is connected to terminal '2'.

When 'S' is connected to a '1', the R-L combination is suddenly put across the voltage of V volt. Let us take the current at closing S as the starting time zero. It is found that current does not reach its max^m value instantaneously but takes some finite time.

We will now investigate the growth of current through such an inductive ckt.

According to Kirchhoff's voltage law

Total voltage applied = voltage across R + voltage to overcome L

$$V = V_R + V_L$$

$$V = iR + L \frac{di}{dt}$$

$$V - iR = L \frac{di}{dt}$$

$$\Rightarrow \frac{di}{V - iR} = \frac{dt}{L}$$

Integrating both sides,

$$\int \frac{di}{V - iR} = \int \frac{dt}{L}$$

Multiplying both sides by $(-R)$, we get

$$\int (-R) \frac{di}{V - iR} = \int \frac{-R}{L} dt$$

Integrating the both sides,

$$\int (-R) \frac{di}{V - iR} = \int \frac{-R}{L} dt$$

$$\Rightarrow \log_e(V - iR) = -\frac{R}{L}t + K$$

Where K is constant of integration whose value can be found from the initial known conditions.

When $t=0, i=0,$

$$\log_e V = K$$

$$\therefore \log_e(V - iR) = -\frac{R}{L}t + \log_e V$$

$$\Rightarrow \log_e \frac{V - iR}{V} = -\frac{R}{L}t$$

$$\Rightarrow V - iR = V e^{-\frac{R}{L}t}$$

$$V - V e^{-\frac{R}{L}t} = iR$$

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$\boxed{i = \frac{V}{R} (1 - e^{-t/\tau})} \quad \text{where } \tau = \text{time constant} = \frac{L}{R} \quad \text{--- (1)}$$

So voltage across the resistor at any instant is

$$V_R = iR$$

$$\Rightarrow \boxed{V_R = V (1 - e^{-t/\tau})}$$

the voltage across the inductor L at any instant is

$$V_L = V - V_R$$

$$= V - V(1 - e^{-t/\tau})$$


$$\boxed{V_L = V e^{-t/\tau}}$$

Now $\frac{V}{R}$ represents the max^m steady value of current

$$i = I_m (1 - e^{-t/\tau})$$

This is an exponential curve whose graph as shown. It is seen that the current is ~~initially~~ rapid at first and then decreases until at $t \rightarrow \infty$, it becomes zero.

but theoretically current does

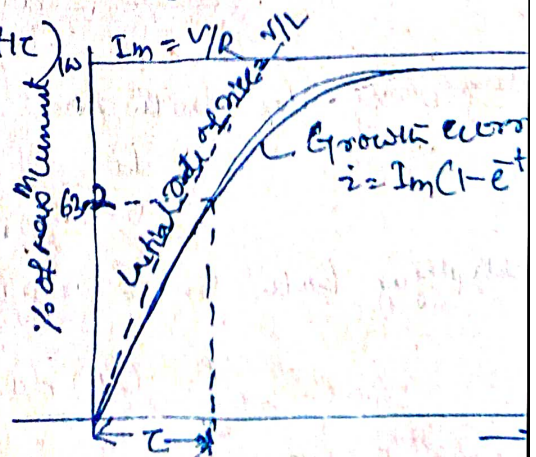

the I_m until infinite time

... the induced EMF ... current $\frac{di}{dt}$...

$$\text{Since } V = iR + L \frac{di}{dt}$$

$$\text{but at } t=0, i=0, V = 0 + L \frac{di}{dt} \quad \frac{di}{dt} = \frac{V}{L}$$

$$\therefore \frac{di}{dt} = \text{initial rate of rise} = \frac{V}{L}$$

Final value of current
The current attains its final value after an infinity of time
Hence $i = i_{\infty}$

$$i = \frac{V}{R} (1 - e^{-t/\tau}) = \frac{V}{R} (1 - e^{-\infty}) = \frac{V}{R} - 0 = \frac{V}{R}$$

Thus, the steady value of current $I_m = \frac{V}{R}$.

Now when time $t = \tau = \text{time constant}$

$$\begin{aligned} \text{then } i &= I_m (1 - e^{-t/\tau}) = I_m (1 - \frac{1}{e}) = I_m (1 - \frac{1}{2.718}) \\ &= 0.632 I_m \end{aligned}$$

Hence the time constant τ of an R-L circuit may also be defined as the time during which the current actually rises to 0.632 of its maximum steady value.

Decay of current in an inductive circuit

When the switch 'S' is connected to point 2, the R-L circuit is short-circuited. So initially when switch is in position 1 for a long time the current in the R-L circuit to be maximum I_m . When the switch moves to position 2, the circuit is disconnected from the supply and V becomes zero.

So the eqn for decay of current when time is found by putting $V=0$

$$0 = iR + L \frac{di}{dt}$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

Integrating both sides, we have

$$\int \frac{di}{i} = -\frac{R}{L} \int dt$$

$$\Rightarrow \log i = -\frac{R}{L} t + k$$

where k is integration constant and it can be found out from initial known condition.

no at the instant of switching off the current is counted from this instant when $t=0$.

$$\log I_m = 0/\tau \Rightarrow K = \log I_m$$

$$\log e^i = -\frac{R}{L}t + \log I_m \Rightarrow \log i = \log I_m - \frac{R}{L}t$$

$$\Rightarrow \log \frac{i}{I_m} = -\frac{R}{L}t \Rightarrow i = I_m e^{-\frac{R}{L}t}$$

$$i = I_m e^{-t/\tau}$$


is an decaying exponential function and its graph is shown

then time $t = \tau$,

$$i = I_m e^{-\tau/\tau}$$

$$= I_m e^{-1} = \frac{I_m}{e}$$

$$= \frac{I_m}{2.718} = 0.37 I_m$$

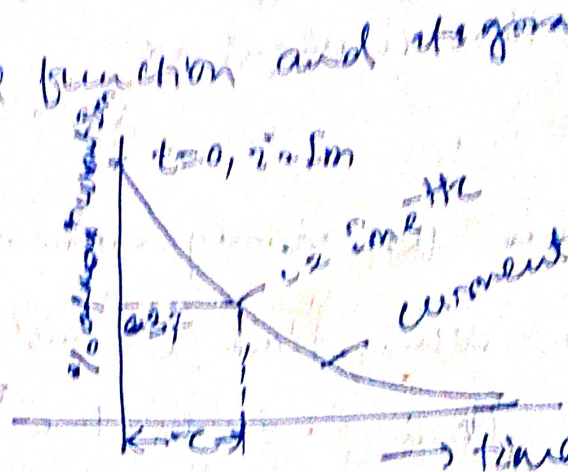

time τ (time constant) at an R-L circuit may also be defined as the time during which current falls to 0.37 or 37% of its max steady value while decaying.

Transient State ($0 < t < \infty$) \rightarrow For growth of current.

It is also called instantaneous state i.e. any time during closing or opening switch.


Initial State - just after closing the switch or just after opening the switch.

Steady State: is a long time after closing or opening switch. In this state current in the conductor is constant with time i.e. $\frac{di}{dt} = 0$.

RC (Growth and decay in RC circuit).

↓ Changing of the capacitor

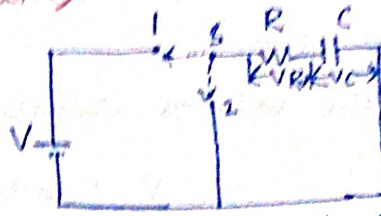Let us consider a circuit containing a capacitor C in series a resistance R connected to a DC supply at voltage V as shown.



When switch 'S' is connected to 1, C is charged but when it is connected to 2, C is short circuited through R and thus discharged. The voltage across C does not rise to V instantaneously but builds up slowly. Changing current is max^m at the start (in when C is uncharged) then it gradually decreases.

- Let V_R - voltage drop across R
- V_C - voltage across C
- q - charge on capacitor
- i - changing current

Now applying the KVL,

$$V = V_R + V_C$$

$$V = iR + V_C \quad \text{but } i = \frac{dq}{dt} \quad q = CV_C$$

$$= R \frac{d(CV_C)}{dt} + V_C$$

$$V - V_C = RC \frac{dV_C}{dt}$$

Now integrating the both sides, we have ✓
 multiply -1 in both sides
 $\int \frac{dV_C}{V - V_C} = \int \frac{dt}{RC}$
 $\int \frac{dV_C}{V - V_C} = - \int \frac{dt}{RC}$

where K is const of integration and it can be found out by the initial known condⁿ.

When $t=0$, $V_C=0$ ✓

So $-\log V = K$

Now putting the K value in the above eqn, we have

$$-\log(V - V_C) = \frac{t}{RC} - \log V$$

$$\log V - \log(V - V_C) = \frac{t}{RC}$$

$$\log \frac{V}{V - V_C} = \frac{t}{RC} \quad \text{or} \quad \log \left(\frac{V - V_C}{V} \right) = - \frac{t}{RC}$$

$$\frac{V - V_C}{V} = e^{-\frac{t}{RC}} \quad \text{as } V - V_C = V e^{-\frac{t}{RC}}$$

The above eqn gives the voltage across the capacitor at any instant -

So the voltage across the resistor at any instant

$$V_R = V - V_C = V - V(1 - e^{-t/RC}) = Ve^{-t/RC}$$

Now $V_C = \frac{q}{C}$ and $v = \frac{dq}{dt}$

$$\text{So } \frac{q}{C} = \frac{d}{dt} (1 - e^{-t/RC})$$

$$q = C(1 - e^{-t/RC})$$

So we found that increase of charge, like potential of capacitor is reached after infinite time.

$$\text{Now } i = \frac{dq}{dt} = C \frac{d}{dt} (1 - e^{-t/RC})$$

$$= \left[\frac{0}{RC} e^{-t/RC} + \frac{e^{-t/RC}}{RC} \right]$$

$$i = \frac{V}{R} e^{-t/RC} = I_m e^{-t/RC}$$

where $I_m = \text{max current} = \frac{V}{R}$

As charging continues, charging current decreases as from the above eqn. It becomes zero when $t \rightarrow \infty$

Different cond in the R-C growth. etc.

(a) At the time $t=0$, just closing the switch, the pd across the capacitor is zero. So $V_C = 0$.

$$V = V_R + V_C \\ = RC \frac{dV_C}{dt} + 0$$


$$\frac{dV_C}{dt} = \frac{V}{RC}$$

is the initial rate of rise of voltage across the capacitor

$$= \frac{dV_C}{dt} = \frac{V}{RC}$$

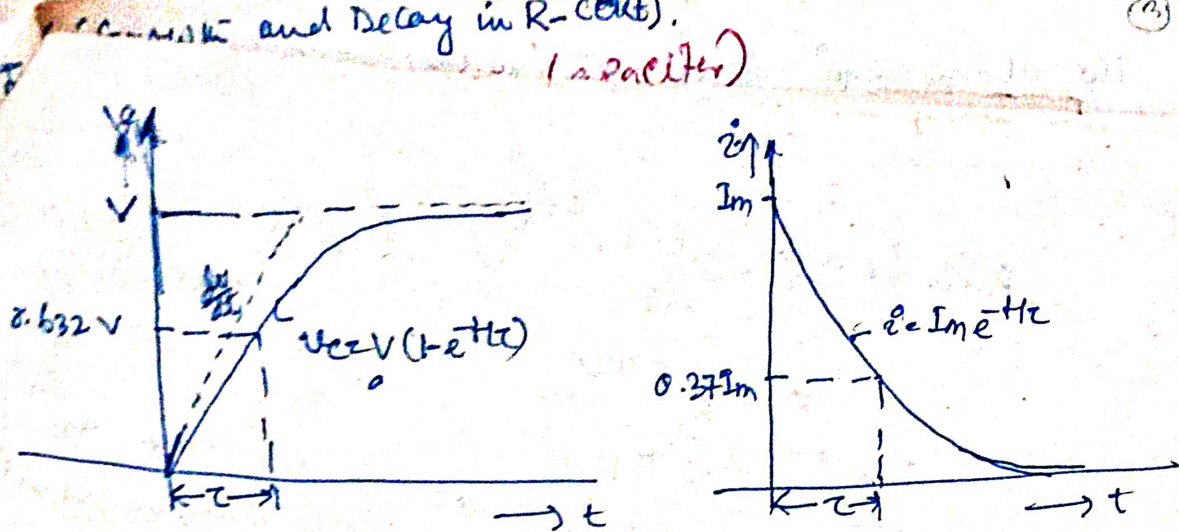(b) When time $t = \text{time constant}$ then resistance $= RC$

$$V_C = V(1 - e^{-t/RC}) = V(1 - e^{-1}) = V(1 - e^{-1})$$



When $t = \infty$, $V_c = V(1 - e^{-\infty/RC}) = V$

When $t = \tau$, $i = I_m e^{-t/RC}$, $I_m e^{-1} = \frac{I_m}{2.718} = 0.37 I_m$

Decay of voltage (Discharge of capacitor)

When switch S is shifted to 2, the capacitor is discharging through R. To begin with discharge current is max^m but then decreases till it is fully discharged.

Since battery is cut out after cut, therefore $V = 0$.

$$V = V_R + V_C$$

$$0 = iR + V_C$$

$$= R \frac{dq}{dt} + V_C$$

$$= RC \frac{dV_C}{dt} + V_C$$

$$\Rightarrow V_C = -RC \frac{dV_C}{dt}$$

$$\frac{dV_C}{V_C} = - \frac{dt}{RC}$$

Integrating the both sides, we have

$$\int \frac{dV_C}{V_C} = - \int \frac{dt}{RC}$$

$$\log V_C = - \frac{t}{RC} + K$$

Where K is const of integration, when $t = 0$, $V_C = V$ i.e., thus

$$\log V = 0 + K$$

$$\log V_C = - \frac{t}{RC} + \log V$$


$$\log \frac{V_C}{V} = - \frac{t}{RC} \Rightarrow \frac{V_C}{V} = e^{-\frac{t}{RC}}$$

$$V_C = V e^{-\frac{t}{RC}} = V e^{-t/\tau} \text{ where } \tau = \text{time constant} = RC$$

Similarly $i = I_m e^{-t/RC}$

A Response of Series R-L-E circuit with DC excitation

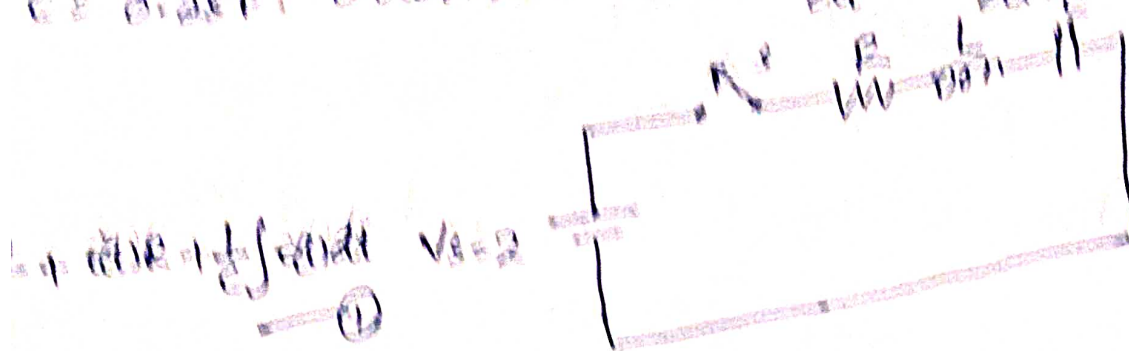In a R-L-E series circuit having $V_s = 2V$, $R = 6\Omega$, $L = 2H$ & $C = 0.25F$. Determine $i(t)$, $\frac{di(t)}{dt}$, $\frac{d^2i(t)}{dt^2}$ and $v(t)$



initially the eqn (1)

$$= 2 \frac{d^2i(t)}{dt^2} + 6 \frac{di(t)}{dt} + \frac{1}{0.25} i(t)$$

$$\Rightarrow \frac{d^2i(t)}{dt^2} + 3 \frac{di(t)}{dt} + 2i(t) = 0 \quad \text{--- (2)}$$

$$p^2 + 3p + 2 = 0$$

The roots of the above eqn,

$$p_1 = -1, p_2 = -2$$

The soln of eqn (2)

$$i(t) = K_1 e^{-t} + K_2 e^{-2t} \quad \text{--- (3)}$$

When switch is closed at $t=0$, $i(0) = 0$

$$V_s = L \frac{di(t)}{dt} \Big|_{t=0} \Rightarrow \frac{di(t)}{dt} = \frac{V_s}{L} = \frac{2}{2} = 1$$

$$i''(t) \quad \frac{d^2i(t)}{dt^2} \Big|_{t=0} + 3 \frac{di(t)}{dt} \Big|_{t=0} + 2i(0) = 0$$

$$\frac{d^2i(0)}{dt^2} + 3 \times 1 + 2 \times 0 = 0 \quad \frac{d^2i(0)}{dt^2} = -3 \text{ A/sec}^2$$

$$i(0) = 0 = K_1 + K_2 \quad \text{--- (4)}$$

$$\frac{di(t)}{dt} = -k_1 e^{-t} - 2k_2 e^{-2t}$$

$$\frac{di(t)}{dt} \Big|_{t=0} = -k_1 - 2k_2$$


$$\Rightarrow 1 = -k_1 - 2k_2 \quad \text{--- (5)}$$

From eqn (4) & (5) $k_1 = 1, k_2 = -1$

$$i(t) = e^{-t} - e^{-2t}$$

Transient Response in RLC parallel circ.

Ex:

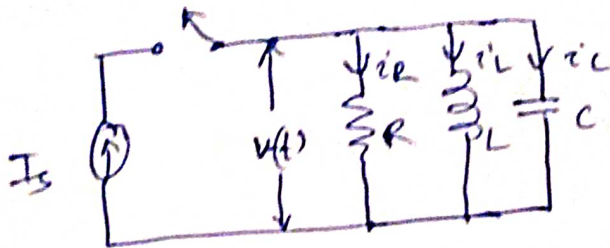

In the above circ. $I_s = 2A, R = \frac{1}{16} \Omega, L = \frac{1}{16} H, C = 4F.$

Determine $v(t), \frac{dv(t)}{dt}, \frac{d^2v(t)}{dt^2}$ and $v(t)$

$$I_s = i_R + i_L + i_C$$

$$= \frac{v(t)}{R} + \frac{1}{L} \int v(t) dt + C \frac{dv(t)}{dt} \quad \text{--- (1)}$$

Differentiating the eqn (1),

$$0 = 16 \frac{dv(t)}{dt} + 16v(t) + 4 \frac{d^2v(t)}{dt^2}$$

$$\Rightarrow \frac{d^2v(t)}{dt^2} + 4 \frac{dv(t)}{dt} + 4v(t) = 0 \quad \text{--- (2)}$$

$$P^2 + 4P + 4 = 0$$

The roots of the eqn $P_1 = -2, P_2 = -2$

The solⁿ of the eqn (2).

$$v(t) = K_1 e^{-2t} + K_2 t e^{-2t} \quad \text{--- (3)}$$

at time $t=0$, $v(0^+) = 0$ \rightarrow as capacitor is shorted

From eqn (1)

$$2 = 0 + 0 + 4 \frac{dv(0^+)}{dt}$$

$$\Rightarrow \frac{dv(0^+)}{dt} = \frac{2}{4} = \frac{1}{2} \text{ V/sec}$$

From eqn (2) $\frac{d^2v(0)}{dt^2} + 4 \frac{dv(0)}{dt} + 4v(0) = 0$

$$\Rightarrow \frac{d^2v(0)}{dt^2} + 4 \times \frac{1}{2} + 4 \times 0 = 0$$

$$\frac{d^2v(0)}{dt^2} = -2 \text{ V/sec}^2$$

From eqn (3), $0 = K_1 + K_2 \times 0$

$$K_1 = 0$$

Diffⁿ in eqn (3) and at $t=0$ we get

$$\frac{dv(t)}{dt} = K_1 e^{-2t} - 2K_2 t e^{-2t}$$

$$-2K_1 + K_2 = \frac{1}{2}$$

$$K_2 = \frac{1}{2}$$

$$v(t) = \frac{1}{2} t e^{-2t}$$

Q. A d.c voltage of 200V is suddenly applied series R-L circuit having $R = 20 \Omega$, $L = 0.2 \text{ H}$. Determine voltage drop across the inductor at the instant switching on and 0.02 sec later.

$$i(t) = \frac{V}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R} = \frac{20}{200} = 0.1$$

$$i(t) = \frac{20}{20} (1 - e^{-0.02 \times 10}) = \frac{0.2}{20} = \frac{1}{100}$$

$$= 8.646 \text{ A}$$

$$V = V_R + V_L \Rightarrow V_L = V - V_R = V - iR$$

$$V_L = 20 - 8.646 \times 20 = 27 \text{ V}$$

A resistance R and $5\mu\text{F}$ capacitor are connected in series across a 100V D.C supply. Calculate the value of R such that the voltage of the capacitor become 50V in 5sec after the circuit is switched on.


solⁿ.

$$V(t) = V(1 - e^{-t/\tau}) \quad \tau = RC$$

$$50 = 100 \left(1 - e^{-\frac{5}{R \times 5 \times 10^{-6}}}\right)$$

$$R = 1.45 \times 10^6 \Omega.$$

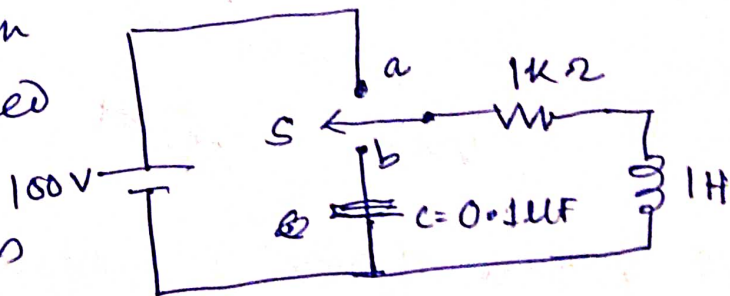Q. In the circuit, when switch S is changed from position a to b at $t=0$. Find values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$



solⁿ:

At position 'a'.

The steady state value of current $i(0^-)$

$$= \frac{100}{1000} =$$

position 'b'

$$1000 i(t) + 1 \frac{d i(t)}{dt} + \frac{1}{0.1 \times 10^{-6}} \int_{-\infty}^t i(t) dt = 0 \quad \text{--- (1)}$$

at $t=0$ $1000 i(0^+) + \frac{d i(0^+)}{dt} + 0 = 0$ $i(0^+) = 0.1$

$$1000 \times 0.1 + \frac{d i(0^+)}{dt} = 0$$

$$\frac{d i(0^+)}{dt} = -100 \text{ A/sec.}$$


Diff. eqn (1) $1000 \frac{d i(t)}{dt} + 1 \frac{d^2 i(t)}{dt^2} + \frac{i(t)}{0.1 \times 10^{-6}} = 0$

at $t=0$ $1000 \times \frac{d i(0^+)}{dt} + \frac{d^2 i(0^+)}{dt^2} + \frac{i(0^+)}{0.1 \times 10^{-6}} = 0$

$$1000 \times (-100) + \frac{d^2 i(0^+)}{dt^2} + \frac{0.1}{0.1 \times 10^{-6}} = 0$$

$$\frac{d^2 i(0^+)}{dt^2} = 10^5 - \frac{1}{10^{-6}} = -9 \times 10^5 \text{ A/sec}^2$$

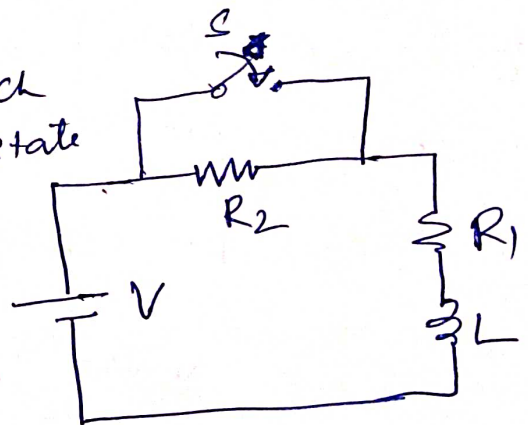Amplitude given at, when switch s is closed at $t=0$, a steady state current having previously been attached. solve for the current as a function of time.



At: Before switch action takes place

$$i(0) = \frac{V}{R_1 + R_2}$$

When switch is closed.

$$V = L \frac{d i}{dt} + R_1 i$$

$$\frac{d i}{dt} + \frac{R_1}{L} i(t) = \frac{V}{L} \quad \text{--- (2)}$$

Solⁿ of eqn (2)

$$i(t) = \frac{V}{R_1} + K e^{-\frac{R_1}{L}t}$$

at time $t=0$, $\frac{V}{R_1+R_2} = \frac{V}{R_1} + K$

$$i(0) = \frac{V}{R_1+R_2}$$

$$K = \frac{V}{R_1+R_2} - \frac{V}{R_1} = -V \cdot \frac{R_2}{R_1(R_1+R_2)}$$

$$i(t) = \frac{V}{R_1} - \frac{V \cdot R_2}{R_1(R_1+R_2)} e^{-\frac{R_1}{L}t}$$


$$i(t) = \frac{V}{R_1} \left(1 - \frac{R_2}{R_1+R_2} e^{-\frac{R_1}{L}t} \right)$$

Q. In the given circuit

find the value of $v_c(t)$

for $t > 0$, Assume

initial condition $v_c(0^-) = 9V$.

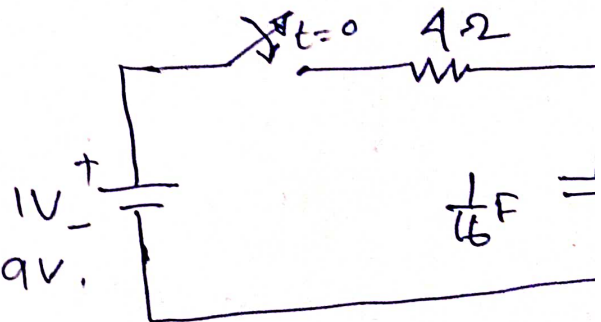

Solⁿ:

$$1 = 4 i(t) + v_c(t) \quad \text{--- (2)}$$

$$v_c(t) = 9 + 16 \int_0^t i(t) dt$$

$$1 = 4 i(t) + 9 + 16 \int_0^t i(t) dt$$

$$4 i(t) + 16 \int_0^t i dt = -8$$

$$i(t) + 4 \int_0^t i(t) dt = -2 \quad \text{--- (1)}$$

Diffⁿ eqn (2)

$$\frac{di(t)}{dt} + 4 i(t) = 0 \quad \text{--- (3)}$$

Solⁿ of the eqn (3)

$$i(t) = K e^{-4t} \quad \text{--- (4)}$$

At from eqn (1)

$$1 = 4 i(0^+) + 9 \Rightarrow i(0^+) = -$$

The impedance of some of the branches changes the

From eqn (4) $i'(0^+) = k$.

$\Rightarrow k = -2$

$i'(t) = -2e^{-4t}$


$$v_c(t) = 9 + 16 \int_0^t i'(t) dt$$

$$= 9 + 16 \int_0^t -2e^{-4t} dt = 9 + 16 \left[\frac{-2e^{-4t}}{-4} \right]_{t=0}^t$$

$$v_c(t) = 9 + 8e^{-4t} - 8 = 1 + 8e^{-4t} \text{ V}$$

Q: In the circuit as shown circuit.

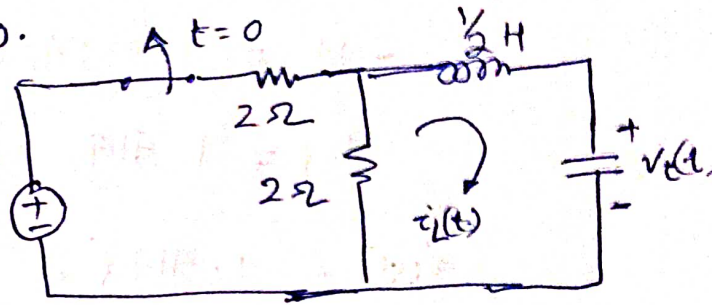is in the steady state with the switch closed. The switch is opened at $t = 0$. Determine $i(t)$ in the circuit.



At steady state with the switch closed. The capacitor behaves as an open circuit, $v_c(0^-) = 2 \text{ V}$, and $i_L(0^-) = 0$. When switch is opened, $v_c(0^+) = v_c(0^-)$ and $i_L(0^+) = i_L(0^-)$

$$2i_L + \frac{1}{2} \frac{di_L(t)}{dt} + \frac{1}{1} \int_0^t i_L(t) dt + v_c(0^-) = 0$$

Diffⁿ the above eqn.

$$2 \frac{di_L}{dt} + \frac{1}{2} \frac{d^2 i_L(t)}{dt^2} + i_L(t) = 0$$

$$\frac{d^2 i_L(t)}{dt^2} + 4 \frac{di_L(t)}{dt} + i_L(t) = 0$$

Char. eqn. $P^2 + 4P + 2 = 0, \Rightarrow P_1 = -3.414$
 $P_2 = -0.586$

$$\text{Sum of } i_L \text{ above } e^{-\lambda t} \quad i_L(t) = k_1 e^{-3.414t} + k_2 e^{-0.586t}$$

$$i_L(0) = 0 \text{ therefore } k_1 + k_2 = 0$$

$$v_L(0^+) = -v_C(0^+) = -2 = L \frac{di_L(0^+)}{dt}$$

$$\frac{di_L(0^+)}{dt} = \frac{-2}{L} = \frac{-2}{\frac{1}{2}} = -4$$

$$\frac{di_L}{dt} = k_1 \times (-3.414) e^{-3.414t} + k_2 (-0.586) e^{-0.586t}$$

$$-4 = -3.414 k_1 - 0.586 k_2$$

$$k_1 = 1.414, \quad k_2 = -1.414$$

$$i_L(t) = 1.414 \left(e^{-3.414t} - e^{-0.586t} \right)$$